


Class 04 MUX / DMUX and Full Adder




June 12, 2014

2


Multiplexer (MUX)

 

S_1	S_0	Y
0	0	D_0
0	1	D_1
1	0	D_2
1	1	D_3

 

S_1	S_0	Y_3	Y_2	Y_1	Y_0
0	0	D_{03}	D_{02}	D_{01}	D_{00}
0	1	D_{13}	D_{12}	D_{11}	D_{10}
1	0	D_{23}	D_{22}	D_{21}	D_{20}
1	1	D_{33}	D_{32}	D_{31}	D_{30}

 

June 12, 2014

3

Multiplexer (MUX)

```
ENTITY mux4sel IS
  PORT(
    s: IN    BIT_VECTOR (1 downto 0);
    d: IN    BIT_VECTOR (3 downto 0);
    y: OUT   BIT);
END mux4sel;

ARCHITECTURE a OF mux4sel IS
BEGIN
  -- Selected Signal Assignment
  MUX4: WITH s SELECT
    y <=    d(0) WHEN "00",
            d(1) WHEN "01",
            d(2) WHEN "10",
            d(3) WHEN "11";
END a;
```



```
ENTITY mux4case IS
  PORT(
    d0, d1, d2, d3: IN BIT; -- data inputs
    s: IN BIT_VECTOR (1 downto 0); -- select inputs
    y: OUT BIT);
END mux4case;



ARCHITECTURE mux4to1 OF mux4case IS
BEGIN
  -- Monitor select inputs and execute if they change
  PROCESS(s)
  BEGIN
    CASE s IS
      WHEN "00"    => y <= d0;
      WHEN "01"    => y <= d1;
      WHEN "10"    => y <= d2;
      WHEN "11"    => y <= d3;
      WHEN others   => y <= '0';
    END CASE;
  END PROCESS;
END mux4to1;
```




June 12, 2014

4


Demultiplexer (DMUX)

  

b. Demultiplexer

 

a. Decoder

 

June 12, 2014

5

Demultiplexer (DMUX) (Cont.)

```

ENTITY dmux8 IS
  PORT(
    s: IN    STD_LOGIC_VECTOR(2 downto 0);
    d: IN    STD_LOGIC;
    y: OUT   STD_LOGIC_VECTOR(0 to 7));
END dmux8;

ARCHITECTURE a OF dmux8 IS
  SIGNAL inputs : STD_LOGIC_VECTOR(3 downto 0);
  BEGIN
    inputs <= d & s;


    WITH inputs SELECT
      y <= "01111111" WHEN "0000",
          "10111111" WHEN "0001",
          "11011111" WHEN "0010",
          "11101111" WHEN "0011",
          "11110111" WHEN "0100",
          "11111011" WHEN "0101",
          "11111101" WHEN "0110",
          "11111110" WHEN "0111",
          "11111111" WHEN others;
  END a;

```

s: selector

"11" & d & "1111" WHEN "0010",


d: signal

 

June 12, 2014

6

Half Adder

 




June 12, 2014

7




Full Adder

A	B	C _{IN}	C _{OUT}	Σ
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

$$\begin{aligned}
 C_{out} &= \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC \\
 &= (\overline{A}B + A\overline{B})C + AB(\overline{C} + C) \\
 &= (A \oplus B)C + AB \\
 \Sigma &= \overline{A}BC + ABC + \overline{A}B\overline{C} + A\overline{B}\overline{C} \\
 &= (\overline{A}B + AB)C + (\overline{A}B + A\overline{B})\overline{C} \\
 &= (\overline{A} \oplus B)C + (A \oplus B)\overline{C} \\
 &= (A \oplus B) \oplus C
 \end{aligned}$$

 


Can't simplify Σ by K-map

   

June 12, 2014

8

 Parallel Binary Adder (Ripple Carry Binary Adder)



$$A_4A_3A_2A_1 = 1101$$

$$B_4B_3B_2B_1 = 0101$$


$$A + B = 10010$$



June 12, 2014

9

Full Adder

 

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY full_add IS
  PORT(
    a, b, c_in : IN      STD_LOGIC;
    c_out, sum : OUT     STD_LOGIC);
END full_add;

ARCHITECTURE adder OF full_add IS
BEGIN
  c_out <= ((a xor b) and c_in) or (a and b);
  sum <= (a xor b) xor c_in;
END adder;

```


$$\begin{aligned}
 C_{out} &= \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC \\
 &= (\overline{A}B + A\overline{B})C + AB(\overline{C} + C) \\
 &= (A \oplus B)C + AB \\
 \Sigma &= \overline{A}BC + ABC + \overline{A}B\overline{C} + A\overline{B}\overline{C} \\
 &= (\overline{A}B + AB)C + (\overline{A}B + A\overline{B})\overline{C} \\
 &= (\overline{A} \oplus B)C + (A \oplus B)\overline{C} \\
 &= ((A \oplus B) \oplus C)
 \end{aligned}$$



June 12, 2014

10

2-Bit Full Adder

 

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

```

```

ENTITY full_add IS
  PORT(
    a, b, c_in : IN      STD_LOGIC;
    c_out, sum : OUT     STD_LOGIC);
END full_add;

```

```

ARCHITECTURE adder OF full_add IS
BEGIN
  c_out <= ((a xor b) and c_in) or (a and b);
  sum <= (a xor b) xor c_in;
END adder;

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY add2par IS
  PORT(
    c0: IN      STD_LOGIC;
    a, b: IN    STD_LOGIC_VECTOR(2 downto 1);
    c2: OUT     STD_LOGIC;
    sum: OUT    STD_LOGIC_VECTOR(2 downto 1));
END add2par;

```

```

ARCHITECTURE adder OF add2par IS
  -- Component declaration
  COMPONENT full_add
  PORT(
    a, b, c_in: IN      STD_LOGIC;
    c_out, sum: OUT     STD_LOGIC);
  END COMPONENT;
  -- Define a signal for internal carry bits
  SIGNAL c : STD_LOGIC_VECTOR(1 downto 1);
  BEGIN
    -- Two Component Instantiation Statements
    adder1: full_add
      PORT MAP ( a    => a(1),
                 b    => b(1),
                 c_in => c0,
                 c_out => c(1),
                 sum   => sum(1));
    adder2: full_add
      PORT MAP ( a    => a(2),
                 b    => b(2),
                 c_in => c(1),
                 c_out => c2,
                 sum   => sum(2));
  END adder;

```

Label is needed

Each component should have different label name

Connect c_out of adder1 to c_in of adder2



June 12, 2014

11

2-Bit Full Adder (Cont.)

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY add4gen IS
  PORT(
    c0: IN  STD_LOGIC;
    a, b: IN  STD_LOGIC_VECTOR(2 downto 1);
    c2: OUT STD_LOGIC;
    sum: OUT STD_LOGIC_VECTOR(2 downto 1));
END add4gen;

```

```

ARCHITECTURE adder OF add4gen IS
  -- Component declaration
  COMPONENT full_add
    PORT( a, b, c_in: IN  STD_LOGIC;
          c_out, sum: OUT STD_LOGIC);
  END COMPONENT;
  -- Define a signal for internal carry bits
  SIGNAL c : STD_LOGIC_VECTOR(2 downto 0);
BEGIN
  c(0) <= c0;
  adder1: full_add PORT MAP (a(1), b(1), c(0), c(1), sum(1));
  adders: <= 2;
  FOR i IN 1 TO 2 GENERATE
    adder: full_add PORT MAP (a(i), b(i), c(i-1), c(i), sum(i));
  END GENERATE;
  c2 <= c(2);
END adder;

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY add2par IS
  PORT(
    c0: IN  STD_LOGIC;
    a, b: IN  STD_LOGIC_VECTOR(2 downto 1);
    c2: OUT STD_LOGIC;
    sum: OUT STD_LOGIC_VECTOR(2 downto 1));
END add2par;

```

```

ARCHITECTURE adder OF add2par IS
  -- Component declaration
  COMPONENT full_add
    PORT(
      a, b, c_in: IN  STD_LOGIC;
      c_out, sum: OUT STD_LOGIC);
  END COMPONENT;
  -- Define a signal for internal carry bits
  SIGNAL c : STD_LOGIC_VECTOR(1 downto 1);
BEGIN
  -- Two Component Instantiation Statements
  adder1: full_add
    PORT MAP ( a    => a(1),
               b    => b(1),
               c_in => c0,
               c_out => c(1),
               sum   => sum(1));
  adder2: full_add
    PORT MAP ( a    => a(2),
               b    => b(2),
               c_in => c(1),
               c_out => c2,
               sum   => sum(2));
END adder;

```



June 12, 2014

12

Full Adder with Unspecified Width

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY addxgen IS
  PORT(
    c0: IN STD_LOGIC;
    a, b: IN STD_LOGIC_VECTOR(width downto 1);
    c_max: OUT STD_LOGIC;
    sum: OUT STD_LOGIC_VECTOR(width downto 1));
END addxgen;

ARCHITECTURE adder OF addxgen IS
  -- Component declaration
  COMPONENT full_add
    PORT(
      a, b, c_in: IN STD_LOGIC;
      c_out, sum: OUT STD_LOGIC);
  END COMPONENT;
  -- Define a signal for internal carry bits
  SIGNAL c : STD_LOGIC_VECTOR(width downto 0);
BEGIN
  c(0) <= c0;
  adders:
  FOR i IN 1 TO width GENERATE
    adder: full_add PORT MAP (a(i), b(i), c(i-1), c(i), sum(i));
  END GENERATE;
  c_max <= c(width);
END adder;

```

Default value
required, but can
be redefined.

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY add16gen IS
  PORT(
    c0: IN STD_LOGIC;
    a, b: IN STD_LOGIC_VECTOR(16 downto 1);
    c16: OUT STD_LOGIC;
    sum: OUT STD_LOGIC_VECTOR(16 downto 1));
END add16gen;

```

Included components
should be in the same
Quartus project as well.

```

ARCHITECTURE adder OF add16gen IS
  COMPONENT addxgen
    GENERIC (width : INTEGER);
  PORT(
    c0: IN STD_LOGIC;
    a, b: IN STD_LOGIC_VECTOR(width downto 1);
    c_max: OUT STD_LOGIC;
    sum: OUT STD_LOGIC_VECTOR(width downto 1));
  END COMPONENT;
BEGIN
  add16 : addxgen
    GENERIC MAP (width => 16)
    PORT MAP (c0, a, b, c16, sum);
END adder;

```

"width" is specified
in GENERIC MAP



June 12, 2014

13

The Procedure to Import VHDL Code to Block Diagram/Schematic File


- The procedure to import a VHDL full-adder to a .bdf file to construct a four-bit full adder:
 1. Create a quartus project with entity name "adder"
 2. Create a new `full_add.vhd` file and save it as a `full_add.bsf` file. (File→Create/Update→Create Symbol File...)
 3. Create a new `adder.bdf` file (the file name is its entity name)
 4. Include `full_add.bsf` file as a component into `adder.bdf`
 5. Pin assignment to complete the design

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```


```
ENTITY full_add IS
  PORT(
    a, b, c_in : IN      STD_LOGIC;
    c_out, sum : OUT     STD_LOGIC;
  END full_add;
```

```
ARCHITECTURE adder OF full_add IS
  BEGIN
    c_out <= ((a xor b) and c_in) or (a and b);
    sum <= (a xor b) xor c_in;
  END adder;
```

full_add.vhd

 

full_add.bsf

 

adder.bdf






June 12, 2014

14

Lab 04

  - Part 1: Design a MUX/DMUX
 - Use Button2-Button0 as the selectors to decide which slide switch among SW7-SW0 is selected to show its status on its corresponding LED. The LEDs that are not selected should be turned off. For example:
 - When Button2 is pushed, the status of SW4 is shown on LEDG4.
 - When Button2 and Button0 are both pushed, the status of SW5 is shown on LEDG5.
- Part 2: Full adder
 - Implement a 4-bit full adder:
 - SW7-4 is the first 4-bit operand, and SW3-0 is the second 4-bit operand.
 - Please show the result on LEDs, where LEDG4 is the carry of the MSB bit, and LEDG3-0 are Σ 3-0, respectively.
 - An LED is on when the corresponding Σ bit is 1.



 


June 12, 2014

15


Pushbutton and Slide Switches

Pin number

 


3 Pushbutton switches:
Not pressed → Logic High
Pressed → Logic Low

Signal Name	FPGA Pin No.
BUTTON [0]	PIN_ H2
BUTTON [1]	PIN_ G3
BUTTON [2]	PIN_ F1

 

10 Slide switches (Sliders):
Up → Logic High
Down → Logic

SW[0]	PIN_ J6	SW[5]	PIN_ J7
SW[1]	PIN_ H5	SW[6]	PIN_ H7
SW[2]	PIN_ H6	SW[7]	PIN_ E3
SW[3]	PIN_ G4	SW[8]	PIN_ E4
SW[4]	PIN_ G5	SW[9]	PIN_ D2

 


June 12, 2014

16


LEDs

Pin number

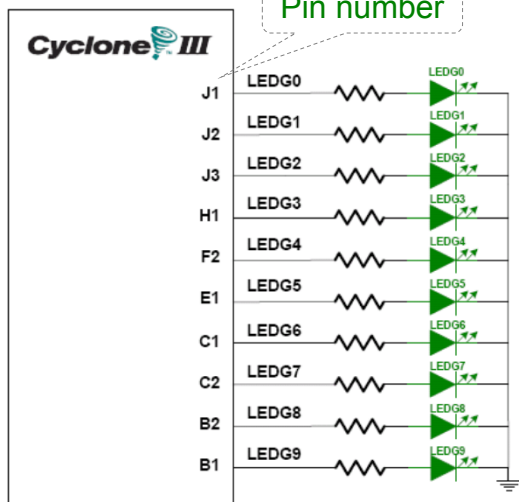

10 LEDs
Output high → LED on
Output low → LED off

Signal Name	FPGA Pin No.
LEDG[0]	PIN_ J1
LEDG[1]	PIN_ J2
LEDG[2]	PIN_ J3
LEDG[3]	PIN_ H1
LEDG[4]	PIN_ F2
LEDG[5]	PIN_ E1
LEDG[6]	PIN_ C1
LEDG[7]	PIN_ C2
LEDG[8]	PIN_ B2
LEDG[9]	PIN_ B1

 


June 12, 2014

17

7-Segment Displays

Pin number
(active-low)

 

Signal Name	FPGA Pin No.						
HEX0_D[0]	PIN_E11	HEX1_D[0]	PIN_A13	HEX2_D[0]	PIN_D15	HEX3_D[0]	PIN_B18
HEX0_D[1]	PIN_F11	HEX1_D[1]	PIN_B13	HEX2_D[1]	PIN_A16	HEX3_D[1]	PIN_F15
HEX0_D[2]	PIN_H12	HEX1_D[2]	PIN_C13	HEX2_D[2]	PIN_B16	HEX3_D[2]	PIN_A19
HEX0_D[3]	PIN_H13	HEX1_D[3]	PIN_A14	HEX2_D[3]	PIN_E15	HEX3_D[3]	PIN_B19
HEX0_D[4]	PIN_G12	HEX1_D[4]	PIN_B14	HEX2_D[4]	PIN_A17	HEX3_D[4]	PIN_C19
HEX0_D[5]	PIN_F12	HEX1_D[5]	PIN_E14	HEX2_D[5]	PIN_B17	HEX3_D[5]	PIN_D19
HEX0_D[6]	PIN_F13	HEX1_D[6]	PIN_A15	HEX2_D[6]	PIN_F14	HEX3_D[6]	PIN_G15
HEX0_DP	PIN_D13	HEX1_DP	PIN_B15	HEX2_DP	PIN_A18	HEX3_DP	PIN_G16