

Class 05

Sequential Logic: Latch




June 5, 2017


2



SR NAND Latch

 

Why called NAND Latch?

 

nS	nR	Q_{t+1}	nQ_{t+1}	Function
/S	/R		/Q _{t+1}	
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q_t	nQ_t	No Change

SR NAND Latch Function Table




June 5, 2017


3



Reset-to-Set Transition

 


 a) Stable in the RESET condition. Set and Reset inputs inactive.




b) Set input activates.


nS	nR	Q_{t+1}	nQ_{t+1}	Function
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q_t	nQ_t	No Change

 

 
c) Change propagates through upper gate. (Either input LOW makes output HIGH.)



 
d) HIGH transfers across feedback line to lower gate, removing active input condition.



 e) Change propagates through lower gate. (Both inputs HIGH, therefore output LOW.)



 f) Feedback transfers LOW to upper gate, completing change to new state.



g) S input goes back to inactive state. SET state held by LOW at inner input of upper gate.




June 5, 2017


4




Set-to-Reset Transition

 

 
a) Stable in the SET condition. Set and Reset inputs inactive.




b) Reset input activates.

 

 c) Change propagates through lower gate. (Either input LOW makes output HIGH.)



 
d) HIGH transfers across feedback line to upper gate, removing active input condition.



e) Change propagates through upper gate. (Both inputs HIGH, therefore output LOW.)



 f) Feedback line transfers LOW to lower gate, completing transition to RESET state.



g) R goes back to inactive level. Latch is stable in new state, held by the 0 on inner input of lower gate.




June 5, 2017


5

Transition from Forbidden State


nS	nR	Q_{t+1}	nQ_{t+1}	Function
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q_t	nQ_t	No Change

 

 
a) Both Set and Reset inputs active. Either input LOW makes output HIGH. Therefore, both outputs HIGH.



 
b) Set and Reset inputs deactivate simultaneously.



 
c) Change propagate through gates simultaneously.



 d) New output levels cross circuit via feedback lines.



 d) New output levels cross circuit via feedback lines.



f) Output logic levels cross circuit via feedback lines. Cycle repeats and circuit oscillates.




June 5, 2017


6

Switch Bouncing

nS	nR	Q_{t+1}	nQ_{t+1}	Function
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q_t	nQ_t	No Change

 

a. Pushbutton

 

b. Toggle




c. Ideal waveform



d. Effect of contact bounce

The contact bounce is shown only on the terminal where contact is being made not broken!

The case of using a pushbutton!

 


June 5, 2017


7

Switch Debouncing

nS	nR	Q_{t+1}	nQ_{t+1}	Function
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q_t	nQ_t	No Change

 

a. Switch debouncer

 

b. Timing diagram




June 5, 2017

8


Gated SR NAND Latch

nS	nR	Q_{t+1}	nQ_{t+1}	Function
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q_t	nQ_t	No Change

SR NAND Latch Truth Table

 


a. Circuit

 

b. ENABLE used as an ON/OFF signal

EN	S	R	Q_{t+1}	nQ_{t+1}	Function
1	0	0	Q_t	nQ_t	No Change
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	1	1	Forbidden
0	X	X	Q_t	nQ_t	Inhibited

Gated NAND Latch Function Table

 

T = equal time interval

c. ENABLE used as a synchronizing signal




June 5, 2017

9




Gated D Latch (Transparent Latch)

 

EN	D	Q_{t+1}	nQ_{t+1}	Function	Comment
1	1	1	0	Set	Transparent
1	0	0	1	Reset	
0	X	Q_t	nQ_t	No Change	Store

Gated D Latch Function Table

 

June 5, 2017




10



Gated D Latch (Cont.)


nS	nR	Q_{t+1}	nQ_{t+1}	Function
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q_t	nQ_t	No Change

SR NAND Latch Truth Table

   

EN	D	Q_{t+1}	nQ_{t+1}	Function	Comment
1	1	1	0	Set	Transparent
1	0	0	1	Reset	
0	X	Q_t	nQ_t	No Change	Store

Gated D Latch Truth Table

 

11

SR NAND Latch with VHDL

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;



ENTITY nand_latch IS
  PORT
  (
    nS : IN STD_LOGIC;
    nR : IN STD_LOGIC;
    Q : OUT STD_LOGIC;
    nQ : OUT STD_LOGIC
  );
END nand_latch;

ARCHITECTURE bdf_type OF nand_latch IS
  SIGNAL wire0 : STD_LOGIC;
  SIGNAL wire1 : STD_LOGIC;
BEGIN

  Q <= wire1;
  nQ <= wire0;
  wire1 <= NOT(nS AND wire0);
  wire0 <= NOT(wire1 AND nR);

END bdf_type;

```

  

12


Edge-Trigger Event


```

ENTITY counter IS
  PORT
  (
    Q: IN STD_LOGIC; -- reset counter
  );
END counter;

ARCHITECTURE a OF counter IS
  SIGNAL cnt: INTEGER RANGE 0 to 10;
BEGIN
  PROCESS(all)
  BEGIN
    IF (cnt > 9) THEN --reset digit
      cnt <= 0;
    ELSIF (Q'EVENT and Q='1') THEN -- Handle counter
      cnt <= cnt + 1;
    END IF;
  END PROCESS;
END a;

```

 

 

June 5, 2017

13


Gated SR NAND Latch for Debouncing

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY counter IS
    PORT
    (
        S, R, Enable : IN STD_LOGIC ; -- Latch's in input
        OnLed: OUT STD_LOGIC
    );
END counter;

ARCHITECTURE a OF counter IS
    SIGNAL Q,nQ : STD_LOGIC; -- debounced control signal
BEGIN

    -- Gated SR NAND latch to debounce pushbutton jitter
    Q <= ((not S) NAND Enable) NAND nQ;
    nQ <= ((not R) NAND Enable) NAND Q;
    OnLed <= Q ;

END a;
```

 


June 5, 2017

14

Two-Digit Counter

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY counter IS
    PORT(S : IN STD_LOGIC; -- Latch's in input);
END counter;
ARCHITECTURE a OF counter IS
    -- count the number of the button pressed
    SIGNAL digit0, digit1: INTEGER RANGE 0 to 16;
BEGIN
    pro0: PROCESS(S)
    BEGIN
        IF (S'EVENT and S='1') THEN -- Handle counter
            -- two-digit counter
            digit0 <= digit0 + 1; -- advance the digit0 by one
            IF(digit0 >= 9) THEN
                digit1 <= digit1 + 1;
                digit0 <= 0;
                IF(digit1 >= 9) THEN -- reset the digit1 to 0 (overflow)
                    digit1 <= 0;
                END IF;
            END IF;
        END IF;
    END PROCESS pro0;
END a;
```

Executed at
the same time

 

15


Lab 05

- **Note: This lab does not allow to use any existing latch modules.**
- Part 1: Gated SR NAND latch
 - Design a gated SR NAND latch.
 - Create a vector waveform file (.vwf) to evaluate the output of the latch.
 - S: count value, binary, simulation period=4us, advanced by 1 every 100ns, **start from 50ns**
 - R: count value, binary, simulation period=4us, advanced by 1 every 200ns, start from 0ns
 - EN: count value, binary, simulation period 4us, advanced by 1 every 2us, start from 0ns
- Part 2: **Gated SR NAND latch application:** Design the on/off pushbuttons with a counter
 - I/O Functions:
 - PushButton2 (S) is to turn on the motor (i.e., LED0: Q).
 - PushButton1 (R) is to turn off motor (i.e., LED0: Q).
 - PushButton0 is to reset the 2-digit BCD (or decimal) counter to 00.
 - Hex1 and Hex0 shows the value of the 2-digit BCD counter.
 - SW0 is to enable/disable the pushbuttons.
 - When SW0 is Logic-High, enable the pushbuttons. Otherwise, the pushbuttons are disabled.
 - The 2-digit BCD counter is advanced by one whenever the motor is turned ON from OFF (**rising-edge trigger**).




16

Pushbutton and Slide Switches

 


3 Pushbutton switches:
Not pressed → Logic High
Pressed → Logic Low

Signal Name	FPGA Pin No.
BUTTON [0]	PIN_ H2
BUTTON [1]	PIN_ G3
BUTTON [2]	PIN_ F1

 

10 Slide switches (Sliders):
Up → Logic High
Down → Logic

SW[0]	PIN_ J6	SW[5]	PIN_ J7
SW[1]	PIN_ H5	SW[6]	PIN_ H7
SW[2]	PIN_ H6	SW[7]	PIN_ E3
SW[3]	PIN_ G4	SW[8]	PIN_ E4
SW[4]	PIN_ G5	SW[9]	PIN_ D2

 


June 5, 2017

17

LEDs

Cyclone III

Pin number

 

10 LEDs
Output high → LED on
Output low → LED off

Signal Name	FPGA Pin No.
LEDG[0]	PIN_J1
LEDG[1]	PIN_J2
LEDG[2]	PIN_J3
LEDG[3]	PIN_H1
LEDG[4]	PIN_F2
LEDG[5]	PIN_E1
LEDG[6]	PIN_C1
LEDG[7]	PIN_C2
LEDG[8]	PIN_B2
LEDG[9]	PIN_B1




June 5, 2017

18

7-Segment Displays

Pin number
(active-low)

 

Signal Name	FPGA Pin No.	Signal Name	FPGA Pin No.	Signal Name	FPGA Pin No.	Signal Name	FPGA Pin No.
HEX0_D[0]	PIN_E11	HEX1_D[0]	PIN_A13	HEX2_D[0]	PIN_D15	HEX3_D[0]	PIN_B18
HEX0_D[1]	PIN_F11	HEX1_D[1]	PIN_B13	HEX2_D[1]	PIN_A16	HEX3_D[1]	PIN_F15
HEX0_D[2]	PIN_H12	HEX1_D[2]	PIN_C13	HEX2_D[2]	PIN_B16	HEX3_D[2]	PIN_A19
HEX0_D[3]	PIN_H13	HEX1_D[3]	PIN_A14	HEX2_D[3]	PIN_E15	HEX3_D[3]	PIN_B19
HEX0_D[4]	PIN_G12	HEX1_D[4]	PIN_B14	HEX2_D[4]	PIN_A17	HEX3_D[4]	PIN_C19
HEX0_D[5]	PIN_F12	HEX1_D[5]	PIN_E14	HEX2_D[5]	PIN_B17	HEX3_D[5]	PIN_D19
HEX0_D[6]	PIN_F13	HEX1_D[6]	PIN_A15	HEX2_D[6]	PIN_F14	HEX3_D[6]	PIN_G15
HEX0_DP	PIN_D13	HEX1_DP	PIN_B15	HEX2_DP	PIN_A18	HEX3_DP	PIN_G16