

Class 06


Sequential Logic: Flip-Flop





June 12, 2017

2


Differences between Latch and Flip-Flop

 

D latch
Level trigger

  

D flip-flop
Edge trigger


 




June 12, 2017

3

Function Table of D Flip-Flop

  

CLK	D	Q_{t+1}	nQ_{t+1}	Function
\uparrow	0	0	1	Reset
\uparrow	1	1	0	Set
0	X	Q_t	nQ_t	Inhibited
1	X	Q_t	nQ_t	Inhibited
\downarrow	X	Q_t	nQ_t	Inhibited


Function table of D flip-flop



June 12, 2017

4

JK Flip-Flop

 


JK flip-flop

nS	nR	Q_{t+1}	nQ_{t+1}	Function
0	0	1	1	Forbidden
0	1	1	0	Set
1	0	0	1	Reset
1	1	Q_t	nQ_t	No Change

SR NAND Latch


EN	S	R	Q_{t+1}	nQ_{t+1}	Function
1	0	0	Q_t	nQ_t	No Change
1	0	1	0	1	Reset
1	1	0	1	0	Set
1	1	1	1	1	Forbidden
0	X	X	Q_t	nQ_t	Inhibited

Gated SR NAND Latch

 

CLK	J	K	Q_{t+1}	nQ_{t+1}	Function
\uparrow	0	0	Q_t	nQ_t	No Change
\uparrow	0	1	0	1	Reset
\uparrow	1	0	1	0	Set
\uparrow	1	1	nQ_t	Q_t	Toggle
0	X	X	Q_t	nQ_t	Inhibited
1	X	X	Q_t	nQ_t	Inhibited
\downarrow	X	X	Q_t	nQ_t	Inhibited


Function table of JK flip-flop

 

June 12, 2017

5

Frequency Divider or Counter

 

	1	2	3	4	5	6	7	8
CLK	1	1	1	1	1	1	1	1
Q ₀	0	1	0	1	0	1	0	1
Q ₁	0	0	1	1	0	0	1	1
Q ₂	0	0	0	0	1	1	1	1



Clock Pulse	Q ₂	Q ₁	Q ₀
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0



June 12, 2017

6

JK Flip-Flop with Asynchronous Inputs

  


	nPRE	nCLR	CLK	J	K	Q _{t+1}	nQ _{t+1}	Function
Sync	1	1	↑	0	0	Q _t	nQ _t	No Change
	1	1	↑	0	1	0	1	Reset
	1	1	↑	1	0	1	0	Set
	1	1	↑	1	1	nQ _t	Q _t	Toggle
Async	0	1	X	X	X	1	0	Preset
	1	0	X	X	X	0	1	Clear
	0	0	X	X	X	1	1	Forbidden
First priority	1	1	0	X	X	Q _t	nQ _t	Inhibited
	1	1	1	X	X	Q _t	nQ _t	Inhibited
	1	1	↓	X	X	Q _t	nQ _t	Inhibited




June 12, 2017

7

T Flip-Flop

 

D flip-flop with an XOR at the input

 

T flip-flop: the output Q toggles on each clock pulse when T is high

CLK	T	Q_{t+1}	Function
↑	0	Q_t	No change
↑	1	$\neg Q_t$	Toggle
0	X	Q_t	Inhibited
1	X	Q_t	Inhibited
↓	X	Q_t	Inhibited

Function table of T flip-flop



June 12, 2017

8

Integer vs. Unsigned STD_LOGIC

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
ENTITY compare4 IS
    PORT(
        a, b : IN INTEGER RANGE 0 TO 15;
        agtb, aeqb, altb : OUT STD_LOGIC);
END compare4;
ARCHITECTURE a OF compare4 IS
    SIGNAL compare : STD_LOGIC_VECTOR(2 downto 0);
BEGIN
    PROCESS (a,b)
    BEGIN
        IF a<b THEN
            compare <= "110";
        ELSIF a=b THEN
            compare <= "101";
        ELSIF a>b THEN
            compare <= "011";
        ELSE
            compare <= "111";
        END IF;
        agtb <= compare(2);
        aeqb <= compare(1);
        altb <= compare(0);
    END PROCESS;
END a;

```

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
USE ieee.std_logic_unsigned.ALL;
ENTITY compare4 IS
    PORT(
        a, b : IN STD_LOGIC_VECTOR(3 downto 0);
        agtb, aeqb, altb : OUT STD_LOGIC);
END compare4;
ARCHITECTURE a OF compare4 IS
    SIGNAL compare : STD_LOGIC_VECTOR(2 downto 0);
BEGIN
    PROCESS (a,b)
    BEGIN
        IF a<b THEN
            compare <= "110";
        ELSIF a=b THEN
            compare <= "101";
        ELSIF a>b THEN
            compare <= "011";
        ELSE
            compare <= "111";
        END IF;
        agtb <= compare(2);
        aeqb <= compare(1);
        altb <= compare(0);
    END PROCESS;
END a;

```




June 12, 2017

9

Signal Attributes and Edges

Attributes of Signal p[0..7]

Attribute	Description	Value
p'HIGH	Upper bound of p	7
p'LOW	Lower bound of p	0
p'LEFT	Left bound of p	0
p'RIGHT	Right bound of p	7
p'LENGTH	Length of p	8

 

June 12, 2017

10

Signal Attributes and Constant with Default Value

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY parity_genx IS
  PORT(
    pe: OUT STD_LOGIC);
END parity_genx;

ARCHITECTURE parity OF parity_genx IS
  CONSTANT width: INTEGER := 8;
  SIGNAL d: STD_LOGIC_VECTOR(0 to width-1);
  SIGNAL p: STD_LOGIC_VECTOR(d'LOW+1 to d'HIGH);
BEGIN
  p(1) <= d(0) xor d(1);


  parity_generate:
  FOR i IN d'LEFT+2 to d'RIGHT GENERATE
    p(i) <= p(i-1) xor d(i);
  END GENERATE;

  pe <= p(d'LENGTH-1);
END parity;




```

Diagram annotations:

- Constant value:** points to `width := 8`
- Default value:** points to `d'LEFT+2` and `d'RIGHT`
- 8-1=7:** points to `width-1` and `d'LENGTH-1`
- 0+2=2:** points to `d'LEFT+2`
- 1:** points to `d(0)`
- 7:** points to `d(1)`
- 7:** points to `p(i-1)`



June 12, 2017

Frequency Divider

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY FrequencyDivider IS
    PORT (
        CLK: IN STD_LOGIC;
        LED: OUT STD_LOGIC);
END FrequencyDivider;

ARCHITECTURE a OF FrequencyDivider IS
    COMPONENT jkff_primitive
    PORT (
        CLK: IN STD_LOGIC;
        Q: OUT STD_LOGIC;
    END COMPONENT;
    SIGNAL Q: STD_LOGIC_VECTOR(25 downto 0);

BEGIN
    -- Frequency Divider
    Q(Q'LOW) <= CLK;
    divider: FOR i IN Q'LOW+1 TO Q'HIGH GENERATE
        divider_unit: jkff_primitive PORT MAP(CLK=>Q(i-1), Q=>Q(i));
    END GENERATE;
    LED <= not Q(Q'HIGH);
END a;
        
```


Map to external 50MHz clock

Imported from `jkff_primitive.bdf` of the same project

1 2
5


Turn the LED on/off every 0.67s
 $1s / (50MHz / 2^{25})$

Generate 25 JK flip-flops

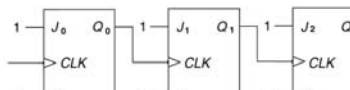




The procedure to import a .bdf design into a VHDL file:

1. Create a `jkff_primitive.bdf` file, and add a JKFF component into this file.
2. Create input and output pins for this JKFF component.
3. In the VHDL file, declare the `jkff_primitive` as its component with only the in/out pins that it wants to use.
4. Generate this component in this VHDL file.



June 12, 2017

FOR Loop and Array

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY FrequencyDivider IS
    PORT (Hex0, Hex1, Hex2, Hex3: OUT STD_LOGIC_VECTOR(0 to 7));
END FrequencyDivider;

ARCHITECTURE a OF FrequencyDivider IS
    CONSTANT DigitValue: INTEGER := 16;
    TYPE MMSS is array (0 to 3) of INTEGER RANGE 0 to DigitValue;
    SIGNAL digits: MMSS;
    TYPE SEVENSEGMENT is array (0 to 3) of STD_LOGIC_VECTOR(0 to 7);
    SIGNAL segments: SEVENSEGMENT;
BEGIN
    -- show 7-segment
    Hex0 <= segments(0);
    Hex1 <= segments(1);
    Hex2 <= segments(2);
    Hex3 <= segments(3);
        
```

Constant with default value 16

Define an integer array

Define an STD_LOGIC_VECTOR array

Map signal to port

Light on "dot" of HEX2

Note:

"101000011000" = x"A18" = o"5030" = b"101000011000"


hexadecimal

binary

octal

```

PROCESS(all)
BEGIN
    FOR i IN 0 TO 3 LOOP
        CASE digits(i) IS
            WHEN 0 => segments(i) <= "00000011"; -- 0
            WHEN 1 => segments(i) <= "10011111"; -- 1
            WHEN 2 => segments(i) <= "00100101"; -- 2
            WHEN 3 => segments(i) <= "00001101"; -- 3
            WHEN 4 => segments(i) <= "10011001"; -- 4
            WHEN 5 => segments(i) <= "01001001"; -- 5
            WHEN 6 => segments(i) <= "11000001"; -- 6
            WHEN 7 => segments(i) <= "00011111"; -- 7
            WHEN 8 => segments(i) <= "00000001"; -- 8
            WHEN 9 => segments(i) <= "00011001"; -- 9
            WHEN others => segments(i) <= "11111111";
        END CASE;
    END LOOP;
    segments(2)(7) <= '0'; -- display "dot"
END PROCESS;
END a;
        
```



June 12, 2017 13

Function

```

LIBRARY ieee;
USE ieee.std_logic_1164.all;
ENTITY FrequencyDivider IS
    PORT (CLK: IN STD_LOGIC;
          Hex0, Hex1, Hex2, Hex3: OUT STD_LOGIC_VECTOR(0 to 7));
END FrequencyDivider;

ARCHITECTURE a OF FrequencyDivider IS
    SIGNAL Ticks : INTEGER;
    TYPE MMSS is array (0 to 3) of INTEGER RANGE 0 to 16;
    SIGNAL TenMiniSecondTicks: INTEGER := 500000;
    SIGNAL digits: MMSS;
    SIGNAL digit;
    FUNCTION PlusOne (a: INTEGER RANGE 0 to 16) RETURN INTEGER IS
        VARIABLE result : INTEGER RANGE 0 to 16;
    BEGIN
        result := a + 1;
        RETURN (result);
    END;

```

Hint:

```

digits(0) <= digit mod 10;
digits(1) <= (digit/10) mod 10;
digits(2) <= (digit/100) mod 10;
digits(3) <= (digit/1000) mod 10;
PROCESS(CLK)
BEGIN
    IF(RISING_EDGE(CLK)) THEN
        Ticks <= Ticks + 1;
        IF(Ticks >= TenMiniSecondTicks-1) THEN
            Ticks <= 0;
            digit <= digit + 1;
        END IF;
    END IF;
END PROCESS;

```

```

BEGIN
    -- Stopwatch
    PROCESS(CLK)
    BEGIN
        IF(RISING_EDGE(CLK)) THEN
            Ticks <= Ticks + 1;
            IF(Ticks >= TenMiniSecondTicks-1) THEN
                Ticks <= 0;
                digits(0) <= PlusOne(digits(0));
                IF(digits(0)>=9) THEN
                    digits(1) <= PlusOne(digits(1));
                    digits(0) <= 0;
                    IF(digits(1)>=9) THEN
                        digits(2) <= PlusOne(digits(2));
                        digits(1) <= 0;
                        IF(digits(2)>=9) THEN
                            digits(3) <= PlusOne(digits(3));
                            digits(2) <= 0;
                            IF(digits(3)>=9) THEN
                                digits(3) <= 0;
                            END IF;
                        END IF;
                    END IF;
                END IF;
            END IF;
        END IF;
    END PROCESS;
END a;

```

Parameters (separated by ;)

Function name


Return value type

Variable (SIGNAL is not allowed in functions)

Value assignment to variable should use :=


Return value


Function call




June 12, 2017 14

DE0 – External Clock



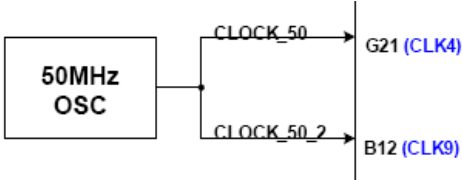


 

15


Lab 06

 - Part 1: Frequency Divider with JK flip-flops or T flip-flops
 - Design a flashing light array with the 50MHz clock
 - LEDG[0..9] is toggled every $2^{[25..34]}$ clock ticks, respectively.
 - E.g., LEDG0 is toggled with 1.49Hz, LEDG1 is toggled with 0.745Hz, and so on.
- Part 2: Design a clock
 - Design a clock with four digits.
 - HEX[3210] represents MM.SS (MM: minutes, SS: seconds), where the “dot” between MM and SS should be always on.
 - Set the initial time to 34.56.



16

DE0 – External Clock

 




June 12, 2017

17




Pushbutton and Slide Switches

Pin number

 

3 Pushbutton switches:
Not pressed → Logic High
Pressed → Logic Low

Signal Name	FPGA Pin No.
BUTTON [0]	PIN_ H2
BUTTON [1]	PIN_ G3
BUTTON [2]	PIN_ F1

 

10 Slide switches (Sliders):
Up → Logic High
Down → Logic

SW[0]	PIN_ J6	SW[5]	PIN_ J7
SW[1]	PIN_ H5	SW[6]	PIN_ H7
SW[2]	PIN_ H6	SW[7]	PIN_ E3
SW[3]	PIN_ G4	SW[8]	PIN_ E4
SW[4]	PIN_ G5	SW[9]	PIN_ D2




June 12, 2017

18




LEDs

Pin number

 

10 LEDs
Output high → LED on
Output low → LED off

Signal Name	FPGA Pin No.
LEDG[0]	PIN_ J1
LEDG[1]	PIN_ J2
LEDG[2]	PIN_ J3
LEDG[3]	PIN_ H1
LEDG[4]	PIN_ F2
LEDG[5]	PIN_ E1
LEDG[6]	PIN_ C1
LEDG[7]	PIN_ C2
LEDG[8]	PIN_ B2
LEDG[9]	PIN_ B1

 


June 12, 2017

19

7-Segment Displays

Pin number
(active-low)

 

Signal Name	FPGA Pin No.						
HEX0_D[0]	PIN_E11	HEX1_D[0]	PIN_A13	HEX2_D[0]	PIN_D15	HEX3_D[0]	PIN_B18
HEX0_D[1]	PIN_F11	HEX1_D[1]	PIN_B13	HEX2_D[1]	PIN_A16	HEX3_D[1]	PIN_F15
HEX0_D[2]	PIN_H12	HEX1_D[2]	PIN_C13	HEX2_D[2]	PIN_B16	HEX3_D[2]	PIN_A19
HEX0_D[3]	PIN_H13	HEX1_D[3]	PIN_A14	HEX2_D[3]	PIN_E15	HEX3_D[3]	PIN_B19
HEX0_D[4]	PIN_G12	HEX1_D[4]	PIN_B14	HEX2_D[4]	PIN_A17	HEX3_D[4]	PIN_C19
HEX0_D[5]	PIN_F12	HEX1_D[5]	PIN_E14	HEX2_D[5]	PIN_B17	HEX3_D[5]	PIN_D19
HEX0_D[6]	PIN_F13	HEX1_D[6]	PIN_A15	HEX2_D[6]	PIN_F14	HEX3_D[6]	PIN_G15
HEX0_DP	PIN_D13	HEX1_DP	PIN_B15	HEX2_DP	PIN_A18	HEX3_DP	PIN_G16